

Resistors and Ohm's Law

Today we will review fundamentals like voltage, current, power, Ohm's Law and Kirchhoff's Laws. The way we think about these concepts will be a little different from the way you thought about them in E&M.

Outline

1	Welcome and Introductions	2
2	Course format	2
3	Electronics in the Lab: Information and Energy	3
4	DC Voltage, Current, and Power	3
5	I-V Relationships and Ohm's Law	4
5.1	Resistors	5
6	Power	6
7	Circuit Diagrams	6
8	Measurement Devices	7
8.1	Voltage Across	7
8.2	Current Through	7

1 Welcome and Introductions

- Your name
- Year
- What are you excited to learn in this class?

2 Course format

- Pre-lab reading and questions, due on Gradescope before each class meeting
 - Pre-lab questions: graded on completion
 - Post-lab questions: graded on correctness
- Class meetings
 - Lecture: about 1 hr
 - Lab activities: main component of course!
- Three midterms
 - In-class, written and hands-on components
 - No final
- Three written reports
 - Two labs (I think 4 and 11) with revision opportunities
 - Digital electronics project write-up
- Open Lab/Office Hours
 - Monday 3:15-4:30pm in SENG 306
- Additional Office Hours by appointment

3 Electronics in the Lab: Information and Energy

sending information
as voltage signals

physical quantities $\rightarrow$ voltages

operations on voltages

low power applications

sensor

signal

power

control:

- motor
- laser
- etc.

GOALS:


① learn how voltages behave in circuits

② use circuits to send signals + control equipment

4 DC Voltage, Current, and Power

Quantity	Physical meaning	Units
Voltage "across"	Electric potential $\hookrightarrow$ <u>difference</u> between points $\hookrightarrow$ <u>relative</u> to some ground (reference pt) related to work required to move charge $V_{12} = -\int_1^2 \vec{E} \cdot d\vec{l}$	Volts (V) $V = J/C$ 0.1 - 30 V in this class
Current "through"	Flow of charges (<u>rate</u>) Through some component	Amp $A = C/s$ $\mu A - mA$ in this class
Power delivered converted dissipated	Energy per time (<u>rate</u>) $P = IV$ energy <u>conversion</u> between different forms (chemical, electrical, thermal, etc)	Watts $W = J/s$ typically mW


5 I-V Relationships and Ohm's Law

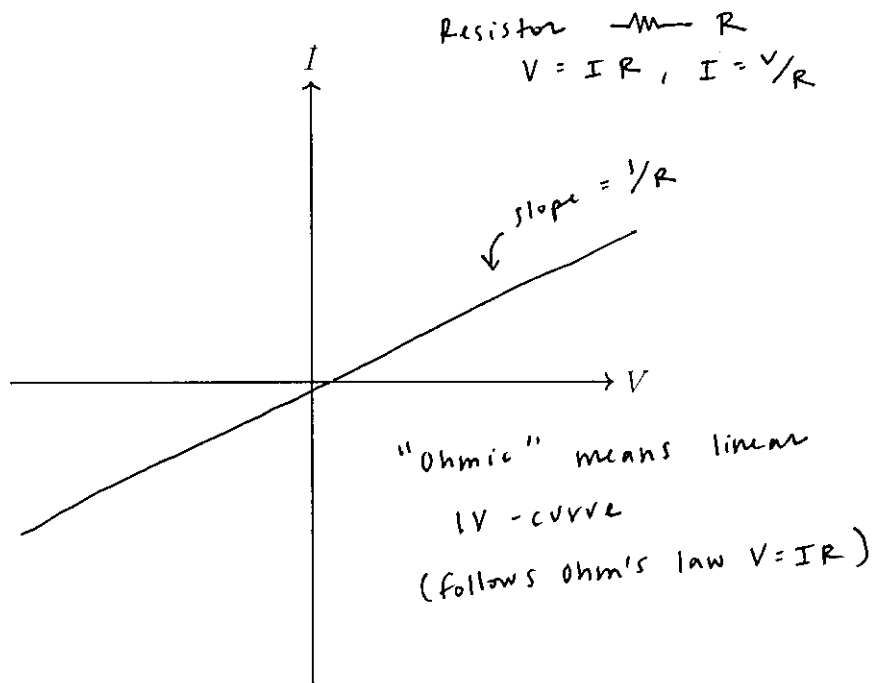


current flow convention:

positive current
 from

$$+V \rightarrow -V$$

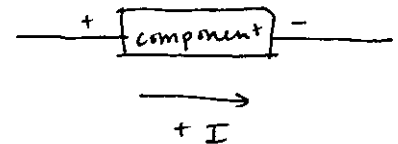

$$\Delta V = V_+ - V_-$$

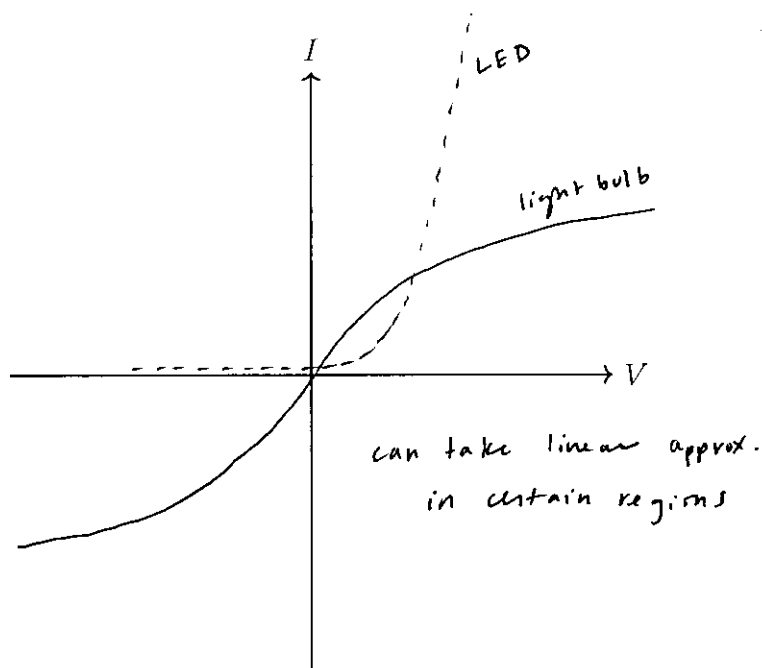

Nonlinear components do
 not have well defined R .



"dynamic resistance"

$$= \frac{dI}{dV} \text{ at some point}$$

ex: diodes
 light bulbs
 transistors

5.1 Resistors

last band gives power

3 Band		1.2MΩ ±20%
4 Band		1KΩ ±5%
5 Band		12.5KΩ ±10%
6 Band		12MΩ ±4% 50ppm/k

$$\underline{10} \underline{2} = 10 \times 10^2 = 1 \text{ k}\Omega$$

$$\underline{125} \underline{2} = 125 \times 10^2 = 12,500 = 12.5 \text{ k}\Omega$$

1st Digit 2nd Digit 3rd Digit Multiplier Tolerance Temp. Coeff.

Black	0	0	0	$\times 10^0$		250 (U)
Brown	1	1	1	$\times 10^1$	±1%	100 (S)
Red	2	2	2	$\times 10^2$	±2%	50 (R)
Orange	3	3	3	$\times 10^3$	±3%	15 (V)
Yellow	4	4	4	$\times 10^4$	±4%	25 (Q)
Green	5	5	5	$\times 10^5$	±0.5%	10 (M)
Blue	6	6	6	$\times 10^6$	±0.25%	10 (L)
Purple	7	7	7	$\times 10^7$	±0.1%	10 (K)
Grey	8	8	8	$\times 10^8$	±0.05%	1 (K)
White	9	9	9	$\times 10^9$		
Gold	-	-	-	$\times 10^{-1}$	±5%	
Silver	-	-	-	$\times 10^{-2}$	±10%	

better

be

right

or

you

great

big

venture

goes

wrong

helpful?


not sure.

power rating typically 250 mW

6 Power

$$P = IV$$

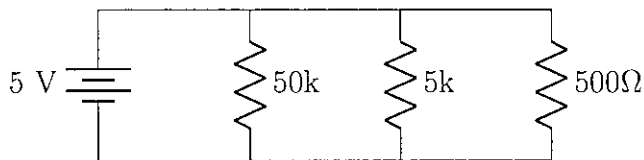resistors: $V = IR \rightarrow P = I^2 R = V^2/R$



- How much current flows through each resistor?
- How much power is dissipated in each resistor?
- Which resistor gets the hottest?
- How much current flows through the battery?


$$I = V/R$$

$$P = IV$$

50k	5k	500
$10^{-4} A$ $= 0.1 mA$	1 mA	10 mA
0.5 mW	5 mW	50 mW
		hottest!


$$\sum I = 0 \text{ in each junction/node}$$
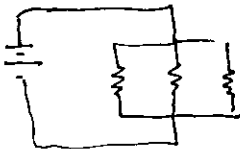
$$\rightarrow I = 0.1 + 1 + 10 = 11.1 mA$$



7 Circuit Diagrams

equivalent!

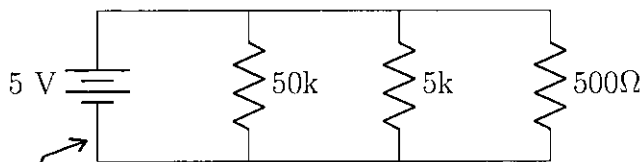

0V point of circuit
"ground"




earth



signal



chassis

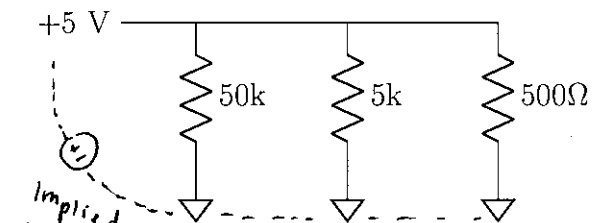

all grounds connected
+ shared w/ implied V-source




$V = 0$

common ground

8 Measurement Devices

8.1 Voltage Across

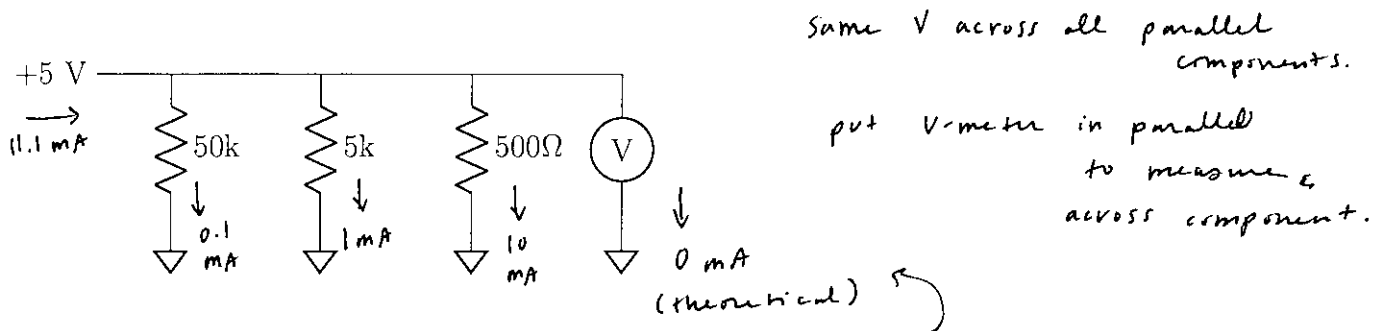

- We want our voltmeter to affect the circuit as little as possible. How much current ideally flows through the meter? How much voltage is ideally across it?


Ideally: 0 A current

otherwise it will affect the total current draw of the circuit

5V measures full voltage

→ ideal V-meter has $R = \infty$!

8.2 Current Through

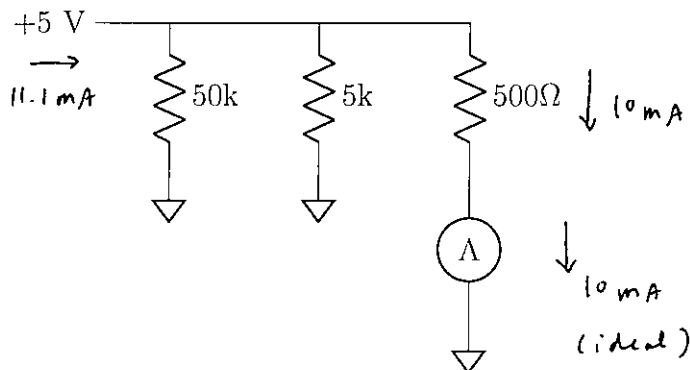

components in series share the same current.

Put the ammeter in series.

- We want our ammeter to affect the circuit as little as possible. How much current ideally flows through the meter? How much voltage is ideally across it?

all current, 0 V

otherwise we would change the component voltage drop!

ideal $R = 0$

